

**Table 1: The Golden Rule**

| S<br>or<br>P      | Circuit | I<br>or<br>Q            | V                       | The law for           |                    | The Equivalent<br><br>Resistor $R_{eq}$<br>or<br>Capacitor $C_{eq}$   |
|-------------------|---------|-------------------------|-------------------------|-----------------------|--------------------|---|
|                   |         |                         |                         | R<br>or<br>C          | Batt<br>ery        |   |
| R<br>in<br>series |         | $I_1 = I_2 = I_3 = I_S$ | $V_1 + V_2 + V_3 = V_S$ | $V = RI$<br>$I = VR$  | $V_S = R_{eq} I_S$ | $R_{eq} = \sum_n R_n$ <p>2 in series</p> $R_{eq} = R_1 + R_2$   |
| C<br>in<br>series |         | $Q_1 = Q_2 = Q_3 = Q_S$ | $V_1 + V_2 + V_3 = V_S$ | $Q = CV$<br>$V = Q/C$ | $Q_S = C_{eq} V_S$ | $C_{eq} = \left[ \sum_n \frac{1}{C_n} \right]^{-1}$ <p>2 in series</p> $C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$ |

**Table 1: The Golden Rule**

| S<br>or<br>P             | Circuit | I<br>or<br>Q            | V                       | The law for           |                    | The Equivalent  |
|--------------------------|---------|-------------------------|-------------------------|-----------------------|--------------------|---|
|                          |         |                         |                         | R<br>or<br>C          | Batt<br>ery        | Resistor $R_{eq}$<br>or<br>Capacitor $C_{eq}$   |
| R<br>in<br>paral-<br>lel |         | $I_1 + I_2 + I_3 = I_S$ | $V = V_S$               | $V = RI$<br>$I = V/R$ | $V_S = R_{eq} I_S$ | $R_{eq} = \left[ \sum_n \frac{1}{R_n} \right]^{-1}$ <p>2 in parallel</p> $R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$ |
| C<br>in<br>paral-<br>lel |         | $Q_1 + Q_2 + Q_3 = Q_S$ | $V_1 = V_2 = V_3 = V_S$ | $Q = CV$<br>$V = Q/C$ | $Q_S = C_{eq} V_S$ | $C_{eq} = \sum_n C_n$ <p>2 in parallel</p> $C_{eq} = C_1 + C_2$   |