

Contents

Ancillary Material

<i>Preface</i>	<i>iii</i>
<i>Contents</i>	<i>v</i>
<i>General Information</i>	<i>vii</i>
<i>Protocol</i>	<i>ix</i>
<i>Lab Errors/Deficiencies Catalog</i>	<i>xiii</i>

Experiments

Electricity & Electromagnetism

<u>1</u>	<i>Basics of Electricity</i>	<i>1</i>
2	<i>Insulators: Capacitance</i>	
	<i>Capacitors in DC and AC Circuits</i>	<i>21</i>
3)	<i>Conductors: Conductance & Resistance</i>	
	<i>Resistors in DC and AC Circuits</i>	<i>41</i>
4	<i>Batteries: Electromotive Force,</i>	
	<i>Internal Resistance and Maximum Current Capability</i>	<i>59</i>
5	<i>Wheatstone's Bridge: Resistors</i>	
	<i>Series and Parallel Arrangements</i>	<i>71</i>
6	<i>Wheatstone's Bridge: Capacitors</i>	
	<i>Series and Parallel Arrangements</i>	<i>81</i>
7	<i>Circuit Analysis I: The Crunching Technique</i>	
	<i>Crunching a 6-Pack of Resistors</i>	<i>89</i>
8)	<i>Circuit Analysis I: The Crunching Technique</i>	
	<i>Crunching a 6-Pack of Capacitors</i>	<i>113</i>

9	<i>Circuit Analysis II a: Kirchhoff's Rules</i>	
	<i>Resistors</i>	137
10	<i>Circuit Analysis II b: Kirchhoff's Rules</i>	
	<i>Capacitors</i>	159
11	<i>Kirchhoff's Rules & Wheatstone's Bridge</i>	
	<i>Resistors</i>	175
12	<i>RC Circuits</i>	
	<i>Charge & Discharge of Capacitors</i>	195
13)	<i>Conductors: Inductance</i>	
	<i>Inductors in DC and AC Circuits</i>	209
14)	<i>R L C - Resonance</i>	
	<i>Inductance</i>	225
15	<i>Frequency Selective Networks</i>	
	<i>(a) High Frequency Selective Network</i>	
	<i>(b) Low Frequency Selective Network</i>	239

Optics

1	<i>Optics - 1</i>	<i>Reflection, Transmission</i>	
		<i>Total Internal Reflection</i>	259
2	<i>Optics - 2</i>	<i>Focal Lengths</i>	
		<i>(i) Converging Lens</i>	
		<i>(ii) Diverging Lens</i>	273
3	<i>Optics - 3</i>	<i>Prism</i>	
		<i>Apex Angle and Refractive Index</i>	287